

Mason Thrall  
CSCI 1510-001  
Lab 1

What can you determine about the little bubble on the output of a NAND gate when you compare the results of its simulation to that of the AND gate with an INVERTER?

**The little bubble does the same thing as an inverter.**  
**The little bubble is another way of drawing an inverter.**  
**An inverter is the same thing as a NOT.**